

# Quiz 5

Phys 296: Summer, 2015

1. We know that  $V = IR$ . Calculate the current in the circuit shown below. (5pt)

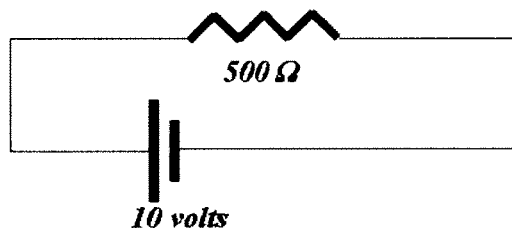


Figure 1

$$V = IR$$

$$I = \frac{V}{R} \quad I = 20 \text{ mA}$$

2. Calculate the equivalent resistance for the combinations of resistors shown below (5pt).


Figure 2(a)



$$1000 \Omega$$

$$R_{eq} = R_1 + R_2$$

Figure 2(b)

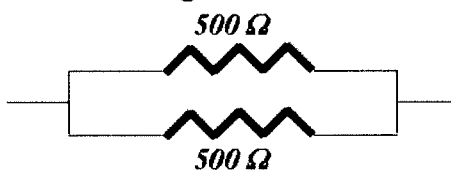

$$250 \Omega$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

3. The temperature coefficient of resistance for a conducting wire is 0.002 per Celsius degree. The electric resistance of the wire is 200  $\Omega$  at 25°C. Calculate the resistance at 0°C. Show derivation. (5pt)

$$(\alpha = 0.002) \quad R(T) = R_0(1 + \alpha T) \quad R(25^\circ) = 200 \Omega$$

$$R_0 = \frac{R(T)}{1 + \alpha T} = 190.48 \Omega \quad R(0^\circ) = R_0$$

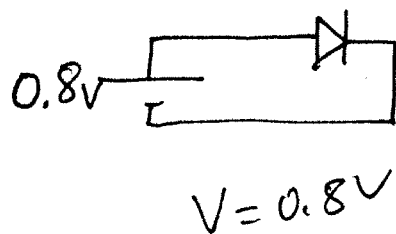4. We know that for a diode  $I = I_0 \left( \exp\left(\frac{qV}{k_b T}\right) - 1 \right)$ . Calculate the current through the diode in the following circuit. (5pt)



$$\frac{q}{k_b T} = 1 \quad I_0 = 1 \mu\text{A}$$

$$I = 1 \mu\text{A} (e^V - 1) = 1.225 \times 10^{-6} \text{ A}$$

$$= 1.225 \mu\text{A}$$