

R-C Circuits

PHYS 296

Your name Key

Lab section _____

PRE-LAB QUIZZES

1. What will we investigate in this lab?

R-C Circuits

2. For the R-C circuit shown in Figure 1 on Page 2, the capacitor is initially not charged and a DC voltage is applied to the circuit at $t = 0$, such that $V(t) = 0$ for $t < 0$ and $V(t) = V_0$ for $t \geq 0$. Obtain the formula for the charge $q(t)$ on the capacitor and the current, $I(t) = dq(t)/dt$, in the circuit.

$$q(t) = CV_0(1 - e^{-t/RC})$$

$$I = \frac{dq}{dt}$$

$$\frac{dq}{dt} = \frac{V_0}{R} e^{-t/RC}$$

$$\text{so } I = \frac{V_0}{R} e^{-t/RC}$$

3. What is the time constant of the R-C circuit?

$$\tau = RC$$

4. What is the current in the circuit at $t = 0$? Does it immediately reach the maximal value?

$$\text{at } t=0 \quad I(0) = \frac{V_0}{R} e^0 = \frac{V_0}{R} \quad \downarrow \text{ YES!}$$

5. What is the magnitude of the current in the circuit?

at $t = RC$:

at $t = \infty$:

$$I(RC) = \frac{V_0}{R} e^{-\frac{RC}{RC}} = \frac{V_0}{eR} \quad I(\infty) \rightarrow 0$$

6. What is the voltage on the capacitor at $t = 0$? Does it immediately reach maximum? \rightarrow NO

$$V(0) = V_0(1 - e^{-0/RC}) = V_0 - V_0 = 0$$

7. What is the magnitude of the voltage $V_C(t)$ on the capacitor?

at $t = RC$:

at $t = \infty$:

$$V(RC) = V_0 - V_0 e^{-1} \quad V(\infty) = V_0$$

8. Draw the $I(t)$ and $V_C(t)$ curves in the following graphs.

